

ASSIGNMENT3

Name:T.B.P.Hariharan

RollNo:2019102019

1.The Netlist for the circuit is shown below

```
.include TSMC_180nm.txt

.param LAMBDA = 0.09u
.param W = {2*LAMBDA}
.global gnd vdd

VDD vdd gnd 1.8

**INPUTS**
Vin1 A gnd pulse(1.8 0 0ns 100ps 100ps 10ns 20ns 0)
Vin2 B gnd pulse(1.8 0 0ns 100ps 100ps 20ns 40ns 0)
Vin3 S gnd 1.8
Vin4 S_bar gnd 0

**INPUT INVERTER**
.subckt cmosinv out in hi lo

.param width_N = {W}
.param width_P = {2*W}

MN out in lo lo CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}
MP out in hi hi CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

.ends cmosinv

**OUTPUT INVERTER**
.subckt varinv out in hi lo pmtr = 3

.param width_N = {pmtr*W}
.param width_P = {(6-pmtr)*W}

MN out in lo lo CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}
MP out in hi hi CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

.ends varinv

**INPUT INVERTER**
xI1 in A vdd gnd cmosinv
xI2 in1 B vdd gnd cmosinv

**OUTPUT INVERTER**
xI3 Y out vdd gnd varinv pmtr = 3
```

```

**PASS TRANSISTORS**

M1 in S out gnd CMOSN W={W} L={2*LAMBDA} AS={5*W*LAMBDA}
PS={10*LAMBDA+2*W} AD={5*W*LAMBDA} PD={10*LAMBDA+2*W}

M2 in1 S_bar out gnd CMOSN W={W} L={2*LAMBDA} AS={5*W*LAMBDA}
PS={10*LAMBDA+2*W} AD={5*W*LAMBDA} PD={10*LAMBDA+2*W}

**TRANSIENT ANALYSIS**

.tran 10ps 100ns

*Calculating delay from A to Y

.measure tran fall
+TRIG v(A) VAL = '0.5*1.8' FALL = 1
+TARG v(Y) VAL = '0.5*1.8' FALL = 1
.measure tran rise
+TRIG v(A) VAL = '0.5*1.8' RISE = 1
+TARG v(Y) VAL = '0.5*1.8' RISE = 1
.measure tran delay_AtoY param = (fall + rise)/2 goal = 0

.control

run

set hcopypscolor = 1
set color0 = white
set color1 = black

set curplottitle = "tbphariharan 2019102019(a)"
plot A
hardcopy 1_A.eps A

set curplottitle = "tbphariharan 2019102019(b)"
plot B
hardcopy 1_B.eps B

set curplottitle = "tbphariharan 2019102019 output(S = 1)"
plot Y
hardcopy 1_Y.eps Y

hardcopy 1_Y.eps Y

.endc

```

$W_p = (6 - k)W$, $W_n = kW$.

For Width(W) = 4 * LAMBDA(least possible value as per design rule checker) , LAMBDA = 0.09 micron .

The minimum average delay is observed to be $1.21463 * 10^{-10}$ seconds when $K = 4$,

$W_n = 4W$, $W_p = 2W$.

Here We are finding delay for $S = 1$ we can find it for $S = 0$ but both give same result, it is sufficient to calculate for $S = 1$ or $S = 0$.


Simulation Results From NGSPICE.

```
Initial Transient Solution
-----
Node          Voltage
----          -
vdd            1.8
a              1.8
b              1.8
s              1.8
s_bar          0
tn             1.128e-08
tn1            1.128e-08
y              1.8
out            1.12794e-08
vin4#branch    0
vin3#branch    0
vin2#branch    0
vin1#branch    0
vdd#branch     -3.07636e-11


Reference value : 6.33425e-08
No. of Data Rows : 20071

Measurements for Transient Analysis
fall           = 1.310454e-10 targ= 1.810454e-10 trig= 5.000000e-11
rise           = 1.118804e-10 targ= 1.026188e-08 trig= 1.015000e-08
delay_atoy     = 1.21463e-10
```


Plots:

 

Input a

 

Input b

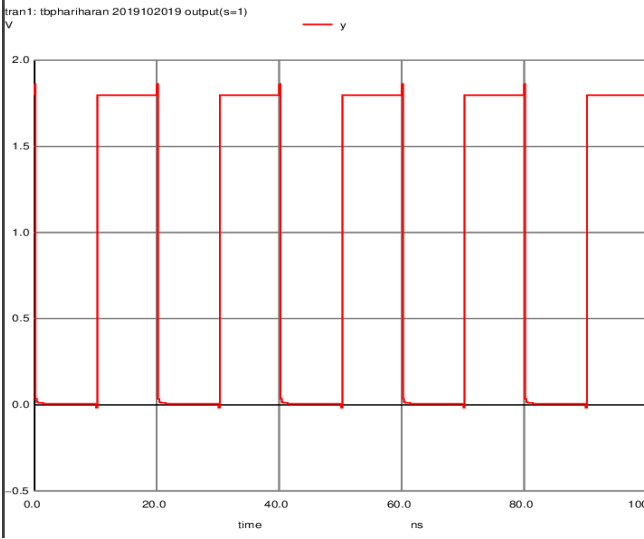

Output Y

2(a). The Shannon Expansion and Circuit diagram are shown

$$f(x_1, x_2, x_3, x_4) = x_1 x_2 + x_1 x_3 + x_1 x_4 + x_2 x_3 + x_2 x_4 + x_3 x_4$$

$$f(x_1, x_2, x_3, x_4) = \bar{x}_1 f(1, x_2, x_3, x_4) + x_1 f(0, x_2, x_3, x_4)$$

$$f(1, x_2, x_3, x_4) = x_2 f(1, 1, x_3, x_4) + \bar{x}_2 f(1, 0, x_3, x_4)$$

$$f(0, x_2, x_3, x_4) = x_2 f(0, 1, x_3, x_4) + \bar{x}_2 f(0, 0, x_3, x_4)$$


$$f(1, 1, x_3, x_4) = x_3 f(1, 1, 1, x_4) + \bar{x}_3 f(1, 1, 0, x_4)$$

$$f(1, 0, x_3, x_4) = x_3 f(1, 0, 1, x_4) + \bar{x}_3 f(1, 0, 0, x_4)$$

$$f(0, 1, x_3, x_4) = x_3 f(0, 1, 1, x_4) + \bar{x}_3 f(0, 1, 0, x_4)$$


$$f(0, 0, x_3, x_4) = x_3 f(0, 0, 1, x_4) + \bar{x}_3 f(0, 0, 0, x_4)$$

 but, $f(0, 0, 0, x_4) = 0$, $f(0, 0, 1, x_4) = x_4$, $f(0, 1, 0, x_4) = x_4$, $f(0, 1, 1, x_4) = 1$, $f(1, 0, 0, x_4) = x_4$,
 $f(1, 0, 1, x_4) = 1$, $f(1, 1, 0, x_4) = 1$, $f(1, 1, 1, x_4) = 1$.



observation: The mux M1 & M2 have same input and select lines.
 one of the mux can be removed.

FINAL CIRCUIT DIAGRAM:

 

2(b).The netlist For the above circuit is shown

```
.include TSMC_180nm.txt

.param LAMBDA = 0.09u
.param Width_N = {4*LAMBDA}
.global gnd vdd

VDD vdd gnd 1.8

Vin1 x1 gnd pulse(1.8 0 0ns 100ps 100ps 10ns 20ns 0)
Vin1_bar x1_bar gnd pulse(0 1.8 0ns 100ps 100ps 10ns 20ns 0)
Vin2 x2 gnd pulse(1.8 0 0ns 100ps 100ps 20ns 40ns 0)
Vin2_bar x2_bar gnd pulse(0 1.8 0ns 100ps 100ps 20ns 40ns 0)
Vin3 x3 gnd pulse(1.8 0 0ns 100ps 100ps 40ns 80ns 0)
Vin3_bar x3_bar gnd pulse(0 1.8 0ns 100ps 100ps 40ns 80ns 0)
Vin4 x4 gnd pulse(1.8 0 0ns 100ps 100ps 80ns 200ns 0)
Vin4_bar x4_bar gnd pulse(0 1.8 0ns 100ps 100ps 80ns 160ns 0)

.subckt mux A B sel sel_bar out

M1 A sel out gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M2 B sel_bar out gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

.ends mux

xM1 vdd x4 x3 x3_bar f1 mux
xM2 x4 gnd x3 x3_bar f2 mux
xM3 vdd f1 x2 x2_bar f3 mux
xM4 f1 f2 x2 x2_bar f4 mux
xM5 f3 f4 x1 x1_bar f mux

.tran 5ps 200ns

.control

set hcopypscolor = 1
set color0 = white
set color1 = black

run

set curplottitle = "tbphariharan-2019102019-2b_x1"
plot x1
```

```

hardcopy x1.eps x1

set curplottitle = "tbphariharan-2019102019-2b_x2"
plot x2
hardcopy x2.eps x2

set curplottitle = "tbphariharan-2019102019-2b_x3"
plot x3
hardcopy x3.eps x3

set curplottitle = "tbphariharan-2019102019-2b_x4"
plot x4
hardcopy x4.eps x4


set curplottitle = "tbphariharan-2019102019-2b_f"
plot f
hardcopy f.eps f

endc


```

Plots :


Inputs :

 


x1

 

x2

 


x3

 

x4

Outputs:

 

$$f = x_1x_2 + x_1x_3 + x_1x_4 + x_2x_3 + x_2x_4 + x_3x_4$$


2(c).

$$f(x_1, x_2, x_3, x_4) = x_1x_2 + x_1x_3 + x_1x_4 + x_2x_3 + x_2x_4 + x_3x_4$$

Observation : If any two of the inputs are **one** the output will be 1. So to get output **one** all the inputs should not be necessarily **one**.

If any three of the inputs are **zero** the output will be 0. So to get output as zero all the inputs should not be necessarily **zero**.

Circuit Diagram Shown Below:

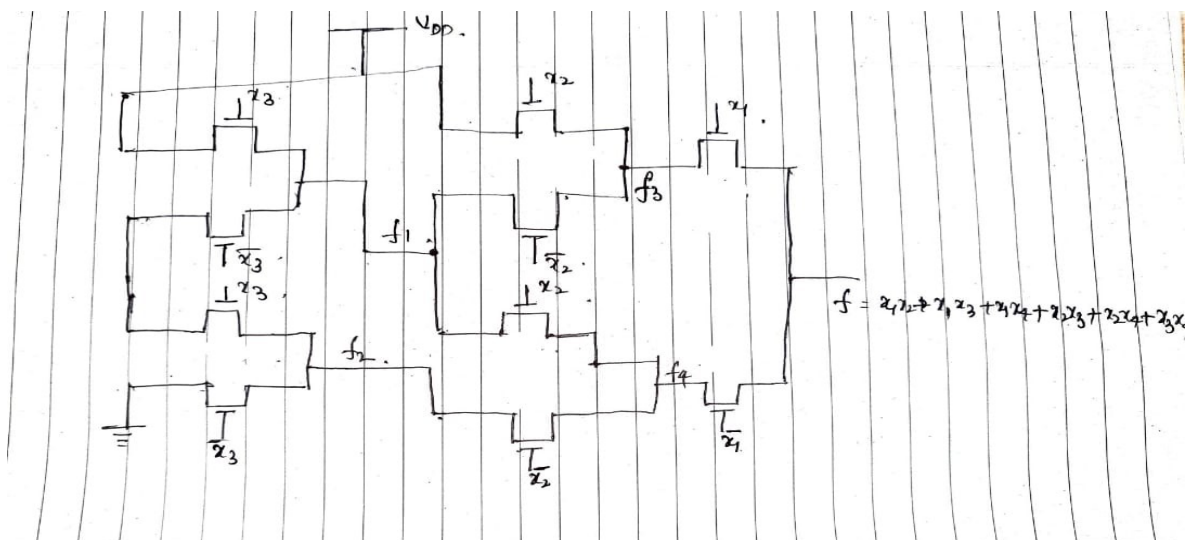

The Paths will be ,

Charging Path:

The Transistors having x_2 and x_1 as gates if $x_2 = 1$, $x_1 = 1$, then f will be **1**.

Discharging Path:

The transistors having $\overline{x_3}, \overline{x_2}, \overline{x_1}$ as gates if $x_3 = 0$, $x_2 = 0$, $x_1 = 0$, then f will be **0**.

```
.measure tran rise
+TRIG V(f) VAL = '0.1*1.2' RISE = 1
+TARG V(f) VAL = '0.9*1.2' RISE = 1

.measure tran fall
+TRIG V(f) VAL = '0.9*1.2' FALL = 1
+TARG V(f) VAL = '0.1*1.2' FALL = 1
.control
```

By adding the above snippet to the netlist in 2(a) we can find the rise and fall time.

From Graph the we get the maximum voltage to be 1.2(approximately).

The rise and fall time are shown below.

```
Measurements for Transient Analysis
rise           = 4.032076e-10 targ= 3.055795e-08 trig= 3.015474e-08
fall           = 3.845555e-11 targ= 1.422150e-10 trig= 1.037594e-10
```

Initial State Final State

The input combinations for charging $(0, 0, 0, 0) = (1, 1, 0, 0)$


The input combinations for discharging $(1, 1, 0, 0) = (1, 0, 0, 0)$

2(d).The buffers have lower charging resistance and increased Drive capacity using this advantage this can decrease the rise time the buffer can be connected after the transistors having gates x_1 and x_2 , thus it decreases the rise time.

3.(a) state table is shown below

State	Inputs ($XR > 0$) ($XR \geq YR$)			Outputs				
	0—	10	11	Subtract	Swap	Select XY	Load XR	Load YR
S_0 (Begin)	S_3	S_1	S_2	0	0	1	1	1
S_1 (Swap)	S_2	S_2	S_2	0	1	0	1	1
S_2 (Subtract)	S_3	S_1	S_2	1	0	0	1	0
S_3 (End)	S_3	S_3	S_3	0	0	0	0	0

 The state diagram for the above state table is shown below.



X represents 0 or 1

S_0 represents begin state.

S_1 represents swap state.

S_2 represents subtract state.

S_3 represents end state(The state where GCD has been computed or it has exited the loop).

3(b). Clearly there are 4 states we require $\lceil \log_2 4 \rceil = 2$, D-FlipFlops are required.

We assign binary codes to the states,

$S_0 = 00$, $S_1 = 01$, $S_2 = 10$, $S_3 = 11$.

Let the output of First and Second D-FlipFlop be D_1 , D_0 respectively.

D_1 , D_0 be the present state of the two FlipFlops.

D_1^+ , D_0^+ be the next state of the two FlipFlops.

The Control Unit's Combinational Logic is derived from the excitation table.


The excitation table is shown below

INPUTS		PRESENT STATE		NEXT STATE		OUTPUTS				
$XR > 0$	$XR \geq YR$	D_1	D_0	D_1^+	D_0^+	SUBTRACT	SWAP	SELECT XY	LOAD XR	LOAD YR
0	X	0	0	1	1	0	0	1	1	1
0	X	0	1	1	0	0	1	0	1	1
0	X	1	0	1	1	1	0	0	1	0
0	X	1	1	1	1	0	0	0	0	0
1	0	0	0	0	1	0	0	1	1	1
1	0	0	1	1	0	0	1	0	1	1
1	0	1	0	0	1	1	0	0	1	0
1	0	1	1	1	1	0	0	0	0	0
1	1	0	0	1	0	0	0	1	1	1
1	1	0	1	1	0	0	1	0	1	1
1	1	1	0	1	0	1	0	0	1	0
1	1	1	1	1	1	0	0	0	0	0

X represents 0 or 1

From the excitation table the control unit's logic can be derived from KMAP


The KMAP for D_1^+ is shown below

 

From the above KMAP,

$$D_1^+ = \overline{(XR > 0)} + (XR \geq YR) + D_0$$

The KMAP for D_0^+ is shown below

 

From the above KMAP,

$$D_0^+ = D_1 D_0 + \overline{(XR \geq YR)} \cdot \overline{(D_0)} + \overline{(XR > 0)} \cdot \overline{(D_0)}$$

From the excitation table,

$$\text{Subtract} = D_1 \cdot \overline{D_0}$$


$$\text{Swap} = \overline{D_1} \cdot D_0$$

$$\text{SelectXY(SXY)} = \overline{D_1} \cdot \overline{D_0}$$

$$\text{Load XR(LXR)} = \overline{D_1} + \overline{D_0}$$

$$\text{Load YR(LYR)} = \overline{D_1}$$

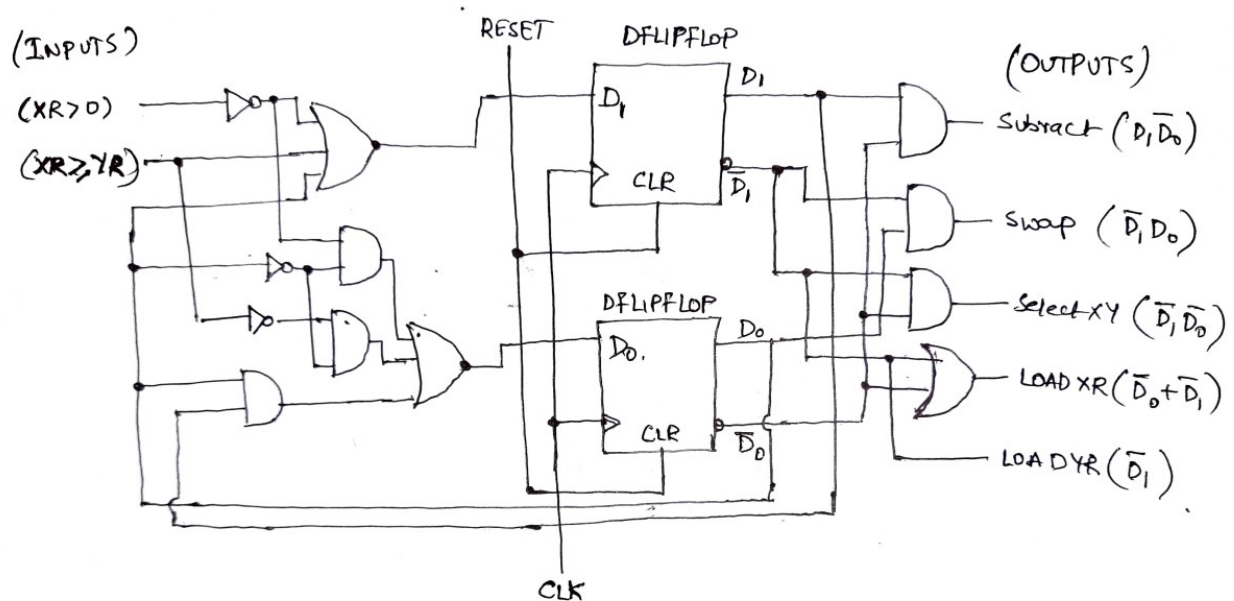The circuit diagram for the **CONTROL UNIT** is shown below



CONTROL UNIT OF GCD PROCESSOR.

3(c).The Above Designed Control Unit is implemented in Verilog HDL.

In this implementation the Four states are encoded with binary codes

S0(begin) = "00", S1(swap) = "01", S2(Subract) = "10", S3(End) = "11".

In this implementation we are not using One Hot Encoding.

Implementation In verilog :

```

module ControlUnit(
    input K1 , K2 , clk , reset,
    output reg subtract = 0 ,
    output reg swap = 0 ,
    output reg selectxy = 0 ,
    output loadxr = 0 ,
    output loadyr = 0,
    output reg [1:0] present = 2'b00 ,
    output reg [1:0] next = 2'b00
);

```

```

    parameter S0 = 2'b00,
               S1 = 2'b01,
               S2 = 2'b10,
               S3 = 2'b11;

```

```

    always @(posedge clk) begin
        if(reset == 1) begin
            present <= S0;
        end
    end

```

```

    always @(present , K1 , K2) begin
        next = S0; //default state
        case(present)
            S0 : begin
                if(K1 == 0)
                    next = S3;
                else if((K1 == 1) & (K2 == 1))
                    next = S2;
                else
                    next = S1;
            end
            S1 : begin
                next = S2;
            end
            S2 : begin
                if(K1 == 0)
                    next = S3;
                else if((K1 == 1) & (K2 == 1))
                    next = S2;
                else
                    next = S1;
            end
            S3 : begin


```

```

                end
            endcase
        end
        always @(*) begin
            subtract = (present == S2) ? 1 : 0;
            swap = (present == S1) ? 1 : 0;
            selectxy = (present == S0) ? 1 : 0;
            loadxr = ((present == S0) | (present == S1) | (present == S2)) ? 1
: 0;
            loadyr = ((present == S0) | (present == S1)) ? 1 : 0;
        end
    endmodule

```

Simulation Results From GTKWave:

 

Where $K1 = (XR > 0)$, $K2 = (XR \geq YR)$, clk is Clock Signal , loadxr is loading the register xr , loadyr is loading the register yr , next[1:0] represents next state of the Control Unit , present[1:0] represents present state of the control unit , reset is reset signal , selectxy is selecting the values x and y. Subtract signal, Swap is Swap signal.

3(d).The behavioral description is shown below

```

module DataPath (
    output wire [5:0] Out,
    output wire K1 , K2, //K1 = (XR > 0) , K2 = (XR >= YR)
    output reg[5:0] AR , BR,
    input wire [5:0] A , B,
    input wire reset , subtract , swap , selectxy , loadxr,
    loadyr , clk
);


    wire [5:0] reg_AR_in , reg_BR_in , reg_BR_out , reg_AR_out , sub_out;
    assign reg_AR_in = subtract ? sub_out : (swap ? reg_BR_out :
        selectxy ? A : reg_AR_out);
    assign reg_BR_in = swap ? reg_AR_out : (selectxy ? B : reg_BR_out);
    always @(posedge clk) begin
        if(reset & loadxr)
            AR <= 0;
        else if (loadxr)
            AR <= reg_AR_in;
    end
    always @(posedge clk) begin
        if(reset & loadyr)
            BR <= 0;
        else if (loadxr)
            BR <= reg_AR_in;
    end

    assign reg_AR_out = AR,
        reg_BR_out = BR,
        Out = reg_BR_out;

    assign sub_out = reg_AR_out - reg_BR_out;
    assign K1 = (reg_AR_out > 0) ? 1 : 0;
    assign K2 = (reg_AR_out >= reg_BR_out) ? 1 : 0;
endmodule

```

Simulation Results From GTKWave

 

The behavioral description of the DataPath Unit is Shown Above.

It is simulated against $X = 1$, $Y = 2$.

“XR_gt_0” represents $XR > 0$, XR_gt_YR represents $XR > YR$. Z is the output of the GCD processor.

3(e).The below description computes GCD and the test bench is shown below.

```
module GCD_behavioral #(parameter W = 16)
(
    input [W - 1:0] AR , BR,
    output[W - 1:0] out
);
    reg [W - 1:0] A , B , out , swap;
    always @(*) begin
        A = AR; B = BR;
        while (B != 0) begin
            if(A < B) begin
                swap = A;
                A = B;
                B = swap;
            end
            A = A - B;
        end
        out = A;
    end
endmodule
```

```

include "behavioralgcd.v"
module gcd_behavioral_tb();
    reg [15:0] AR , BR , AR1 , BR1;
    wire [15:0] out , out1;

    GCD_behavioral#(16) gcd_unit(AR , BR , out);

    initial begin
        $dumpvars(0 , gcd_behavioral_tb);
        $dumpfile("dump.vcd");
    end

    initial begin
        AR = 27; BR = 19;

        #10;

        $display("gcd(27 , 19) = %x",out);

        $finish;
    end

    GCD_behavioral#(16) gcd_unit1(AR1 , BR1 , out1);

    initial begin
        AR1 = 24; BR1 = 16;


        #10;

        $display("gcd(24 , 16) = %x",out1);

        $finish;
    end
end

```

Simulation Results From GTKWave

 

'AR' , 'BR' , 'AR1' , 'BR1' , 'out' , 'out1' are all 16 bit registers(It is a default value but it can be changed to either 32 or 64-bit with the help of parameter W).

'AR' represents the number 27 , 'BR' represents the number 19 , 'out' represents $\text{gcd}(27 , 19) = 1$, clearly the output of 'out' signal is 1.

'AR1' represents the number 24 , 'BR1' represents the number 16 , 'out1' represents $\text{gcd}(24,16) = 8$, clearly the output of 'out1' is 8.